

MID-TERM EXAMINATION

Course: Introduction to Computer Hardware (20CTT1-B)

Time: 75 minutes

Term: 3 – Academic year: 2021-2022


Lecturer(s): **Dinh Dien**

Student name:

Student ID:

(Notes: Neither books nor laptops, phones allowed)

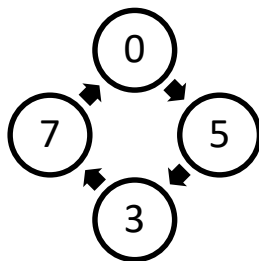1. Design a circuit that will tell whether a given month has 31 days in it. The month is specified by a 4-bit input A3:0. For example, if the inputs are 0002, the month is February, and if the inputs are 1011, the month is November. The circuit output Y should be HIGH only when the month specified by the inputs has 30 days in it. Write the simplified equation, and draw the circuit diagram using a minimum number of gates.
2. A multiplier circuit employing Booth algorithm is used to multiply two numbers -9 (multiplicand) and 6 (multiplier) expressed in 2's complement binary notation. Show the Booth recording for the multiplier and calculate the product by using Booth algorithm.
3. Design a 7-seg decoder using common Anode 7-seg for binary code 10, 11, 12, 13, 14, 15 to F, d, A, H, L, P. Don't care binary code from 0 to 9.
4. Design a synchronous up counter using JK-FlipFlops. The value of counter is shown in following diagram



Note: All problems need explain in your design

--END--